Table of Contents

Close and Clear command and the workspace windows Part 1: Wheatstone Bridge Part 2: Semiconductor	1 1
Tall 2. Schileonadeoi	_
%{ Christopher Simon	
<pre>HW 9: Wheatstone Bridge and Semiconductor %}</pre>	

Close and Clear command and the workspace windows

Part 1: Wheatstone Bridge

```
% Resistor Values
R1 = 120;
R2 = 120;
R3 = 250;
R4 = 250;
% The variable resistance value
RV = linspace(0,500);
% Prompt for an input voltage
V = input('Enter a battery voltage from 5 to 20 volts: ');
if(V < 5 | V > 20)
    error('Please enter a value in between 5 and 20!');
% Calculate both voltages for the two different variables
Vab1 = V * ((R2 ./ (RV + R2)) - (R4 ./ (R3 + R4))); % Variable Resistor, R1
Vab2 = V * ((RV ./ (R1 + RV)) - (R4 ./ (R3 + R4))); % Variable Resistor, R2
% Plot both variable resistor graphs vs the voltage across
% NumberTitle off hides the Figure number in the window title
figure('Name','Variable Resistance','NumberTitle','off');
subX = 2;
subY = 1;
subplot(subX, subY, 1); % 2x1 Grid for Subplots. Subplot 1
plot(RV, Vab1);
title('Variable R1 vs Voltage across A and B');
```

```
xlabel('R1 (Ohms)');
ylabel('vAB (Volts)');
subplot(subX, subY, 2); % 2x1 Grid for Subplots. Subplot 2
plot(RV, Vab2);
title('Variable R2 vs Voltage across A and B');
xlabel('R2 (Ohms)');
ylabel('vAB (Volts)');

Error using input
Cannot call INPUT from EVALC.

Error in homework9 (line 23)
V = input('Enter a battery voltage from 5 to 20 volts: ');
```

Part 2: Semiconductor

```
% Clear the console from part 1
                     % Saturation Current
Is = 10.^{(-12)};
q = 1.6 .* 10.^{(-19)}; % Elementary Charge Value
k = 1.38 .*10^(-23); % Boltzmann's Constant
% Prompt for a voltage drop from the user
Vd = input('Enter a voltage drop from 0.2 and 3.0 volts: ');
if(Vd < 0.2 | Vd > 3.0)
    error('Please enter a value in between 0.2 and 3.0!');
end
% Calculate the current
[Vd, Y] = meshgrid(0:.025:Vd, 290:2:320);
I = Is .* ((exp((q*Vd) ./ (k*Y)) - 1));
% Generate a 3D grid from the given values
figure('Name','Semiconductor','NumberTitle','off');
mesh(Vd, Y, I);
title('Voltage Drop vs Temperature vs Current');
xlabel('Voltage Drop (Volts)');
ylabel('Temperature (Kelvin)');
zlabel('Current (Amps)');
```

Published with MATLAB® R2014b