
Table of Contents

.....	1
Clear command and the workspace windows	1
Voltage and Resistor values	1
Calculations	1

```
%{  
    Christopher Simon  
    HW 8: Kirchhoff's Law  
}%
```

Clear command and the workspace windows

```
clc;  
clear;
```

Voltage and Resistor values

```
v = [30; 5; -25];  
r = [  
    11 -3  0;  
    -3  6 -1;  
     0 -1  3  
    ];
```

Calculations

Calculate the current using right division on the matrix

```
i = r \ v;  
  
% Get each of the loop currents from the matrix  
i1 = i(1);  
i2 = i(2);  
i3 = i(3);  
fprintf('The current in loop 1 is %.2f amps\n', i1);  
fprintf('The current in loop 2 is %.2f amps\n', i2);  
fprintf('The current in loop 3 is %.2f amps\n\n', i3);  
  
% Calculate the average current  
iAvg = mean(i);  
fprintf('The average current is %.2f amps\n\n', iAvg);  
  
% Calculate the equivalent resistance using left division on the matrix  
eqRes = v / iAvg;  
fprintf('The equivalent resistance for loop 1 is %.2f ohms\n', eqRes(1));  
fprintf('The equivalent resistance for loop 2 is %.2f ohms\n', eqRes(2));  
fprintf('The equivalent resistance for loop 3 is %.2f ohms\n', eqRes(3));
```

*The current in loop 1 is 3.00 amps
The current in loop 2 is 1.00 amps
The current in loop 3 is -8.00 amps*

The average current is -1.33 amps

*The equivalent resistance for loop 1 is -22.50 ohms
The equivalent resistance for loop 2 is -3.75 ohms
The equivalent resistance for loop 3 is 18.75 ohms*

Published with MATLAB® R2014b